6.2202 class notes

Erich Trieschman

2026 Fall semester

Contents

1 Circuit review 1

2 Power 2

3 Three-phase and per unit 2

4 Power flow and admittance matrices 2

5 Power line models 2

6 Magnetism and magnetic circuits 3

7 Transformers 3

8 Machines 4

1 Circuit review

Laws. KCL: at every node, $\sum$(currents in) = $\sum$(currents out). KVL: around every closed loop, $\sum V = 0$.

Phasors. Sinusoid $v(t) = V_{max}\cos(\omega t + \phi)$. Positive ϕ shifts the curve left, so the waveform occurs earlier. RMS value: $\tilde{V} = V_{rms} = V_{max}/\sqrt{2}$. Power engineering reports V_{rms}, not V_{max}; state which you use. $v(t) = \mathrm{Re}\{\tilde{V}\cos(\omega t + \phi) + j\tilde{V}\sin(\omega t + \phi)\} = \mathrm{Re}\{\tilde{V}e^{\omega t + \phi}\}$. $Ve^{\omega t + \phi} = Ve^{\phi}e^{\omega t}$; phasor drops $e^{\omega t}$ and is $V = \tilde{V}\angle\phi$, a complex number with RMS magnitude and angle ϕ. $j = \sqrt{-1} = 1\angle 90°$, and $1/j = -j$. Rectangular $\iff$ polar: $a + jb = \sqrt{a^2 + b^2}\angle \mathrm{atan2}(b, a)$, and $r\angle\theta = r\cos\theta + jr\sin\theta = re^{j\theta}$. Add and subtract in rectangular. Multiply and divide in polar: $(r_1\angle\theta_1)(r_2\angle\theta_2) = r_1r_2\angle(\theta_1 + \theta_2)$, $(r_1\angle\theta_1)/(r_2\angle\theta_2) = (r_1/r_2)\angle(\theta_1 - \theta_2)$. Conjugate: $(r\angle\theta)^* = r\angle(-\theta)$.

Elements. Sign convention: I is defined entering the + terminal of passive V. Impedance $Z = R + jX$ [Ω], with resistance R and reactance X. Polar: $Z = |Z|\angle\theta$, $|Z| = \sqrt{R^2 + X^2}$, $\tan\theta = X/R$. Admittance $Y = 1/Z = G + jB$ [S], with conductance G and susceptance B; in polar $Y = (1/|Z|)\angle(-\theta)$. Ohm's law: $V = IZ$, or $I = VY$. With $V = \tilde{V}\angle\phi_V$ and $I = \tilde{I}\angle\phi_I$, $\theta = \phi_V - \phi_I$. Inductor L: $v = L\,di/dt$, so $X_L = \omega L$. Capacitor C: $i = C\,dv/dt$, so $X_C = -1/(\omega C)$. Inductive ("lag"): $\theta > 0$, $\phi_I < \phi_V$, current occurs after voltage. Capacitive ("lead"): $\theta < 0$, $\phi_I > \phi_V$, current occurs before voltage.

Solving. Series: $Z_{eq} = Z_1 + Z_2 + \ldots$; same current through each. Parallel: $Y_{eq} = Y_1 + Y_2 + \ldots$, or $Z_{eq} = Z_1Z_2/(Z_1 + Z_2)$ for two; same voltage across each. Voltage divider (series): $V_2 = V \cdot Z_2/(Z_1 + Z_2)$. Current divider (parallel): $I_2 = I \cdot Z_1/(Z_1 + Z_2)$. Thevenin: a source V_{Th} in series with Z_{Th}. V_{Th} is the open-circuit voltage at the terminals. Z_{Th} is the impedance seen at the terminals with independent sources zeroed (voltage source → short, current source → open), or $Z_{Th} = V_{oc}/I_{sc}$. Norton: a current source $I_N = V_{Th}/Z_{Th}$ in parallel with $Z_N = Z_{Th}$. $v = V_{\mathrm{TH}} + R_{\mathrm{TH}}i$.

Transients. First-order RC or RL circuit with a DC source: $x(t \geq 0) = x(\infty) + [x(0^+) - x(\infty)]\,e^{-t/\tau}$ for any voltage or current x. Time constant $\tau = R_{Th}C$ (RC) or L/R_{Th} (RL), with R_{Th} the Thevenin resistance seen by v_C or i_L. v_C and i_L cannot jump: $x(0^+) = x(0^-)$. $x(\infty)$: capacitor open, inductor short. Any other variable at 0^+: redraw with C as a voltage source $v_C(0^+)$ (or L as a current source $i_L(0^+)$) and solve. Origin: particular solution (steady state) plus homogeneous $Ae^{-t/\tau}$, with A set by $x(0^+)$. Power absorbed by any element: $p(t) = v(t)\,i(t)$. Stored energy is $w(t) = \int_0^t p(t)\,dt = \int v(t)\,i(t)\,dt$. Capacitor: $i(t)\,dt = C\,dv$, so $w(t) = \int v(t)\,C\,dv = \frac{1}{2}Cv(t)^2$. Inductor: $v(t)\,dt = L\,di$, so $w(t) = \int L\,i(t)\,di = \frac{1}{2}Li(t)^2$.

2 Power

Definitions. Complex power $S = VI^*$ [VA]; S is power absorbed by the element. $S = P + jQ$, with real power P [W] and reactive power Q [VAr]. Polar: $S = \tilde{V}\tilde{I}\angle\theta$, where $\theta = \phi_V - \phi_I$. So $P = \tilde{V}\tilde{I}\cos\theta$, $Q = \tilde{V}\tilde{I}\sin\theta$, $|S| = \tilde{V}\tilde{I}$, and $Q = P\tan\theta$. Power factor pf $= \cos\theta = P/|S|$. $\cos\theta$ loses the sign of θ, so a pf is stated lagging or leading. Lagging: $\theta > 0$, inductive, $Q > 0$, absorbs Q. Leading: $\theta < 0$, capacitive, $Q < 0$, supplies Q. Single element: $S = \tilde{I}^2 Z = \tilde{V}^2 Y^*$.

Derivation of P. $p(t) = v(t)\,i(t) = V_{max}I_{max}\cos(\omega t + \phi_V)\cos(\omega t + \phi_I)$. By $\cos\alpha\cos\beta = \frac{1}{2}[\cos(\alpha-\beta) + \cos(\alpha+\beta)]$, $p(t) = \frac{1}{2}V_{max}I_{max}[\cos(\phi_V - \phi_I) + \cos(2\omega t + \phi_V + \phi_I)]$. The first term is constant; the second averages to zero. So $P = \frac{1}{2}V_{max}I_{max}\cos\theta = \tilde{V}\tilde{I}\cos\theta$.

Load to element. A problem states a load as $|S|$ (or P) and a pf, lagging or leading. $\theta = \pm\arccos(\text{pf})$, positive if lagging. As a current: $I = (S/V)^*$, so $\tilde{I} = |S|/\tilde{V}$ and $\phi_I = \phi_V - \theta$. As an impedance: $Z = \tilde{V}^2/S^*$.

Conservation. $\sum S = 0$ at a node and P and Q balance separately. Power-factor correction: given P, pf θ_1, bus $V = \tilde{V}\angle 0$, target θ_2; find C in parallel with the load. $S_L = P + jP\tan\theta_1$; $S_C = |V|^2 Y^* = -j\omega C\tilde{V}^2$; $S_{src} = S_L + S_C = P + j(P\tan\theta_1 - \omega C\tilde{V}^2)$. Target: $Q_{src} = P\tan\theta_2$, since $Q = P\tan\theta$ and P is unchanged.

3 Three-phase and per unit

Definitions. Balanced: phase b is phase a $\angle -120°$, phase c is phase a $\angle +120°$, for every voltage and current; solve phase a only. Balanced line currents sum to zero, so the neutral carries no current and may be omitted. V_{ln}: phase to neutral, e.g. V_{an}. V_{ll}: phase to phase, $V_{ab} = V_{an} - V_{bn} = \sqrt{3}\,V_{an}\angle +30°$. Voltage ratings are V_{ll} unless stated. Relationship holds for both connection types. Line current: in a conductor between source and load (I_a). Phase current: in one load element; equals the line current in Y (I_{ab} in Δ).

Connections. Y: element between phase and neutral; element voltage V_{ln}, element current $I_a = V_{an}/Z_Y$. Δ: element between two phases; element voltage V_{ll}, element current $I_{ab} = V_{ab}/Z_\Delta$. Δ line current: $I_a = I_{ab} - I_{ca} = \sqrt{3}\,I_{ab}\angle -30°$. Δ to Y: $Z_Y = Z_\Delta/3$ gives the same line currents.

Solving. Convert every Δ to Y and every V_{ll} to $V_{ln} = V_{ll}/\sqrt{3}\angle -30°$. Draw phase a: source V_{an}, series source and line impedances, Y-equivalent load, neutral return (zero impedance, present or not); shunt elements line to neutral. A load given as $|S_{3\phi}|$ (or P) and a pf at load voltage V_{ll}: $S_\phi = |S_{3\phi}|\angle\theta/3 = P/(3\text{pf})\angle\theta$ with θ from pf; $Z_Y = \tilde{V}_{ln}^2/S_\phi^*$.

Power. $S_{3\phi} = 3V_{an}I_a^* = \sqrt{3}\,\tilde{V}_{ll}\tilde{I}_{line}\angle\theta$. Y: $|S|_{3\phi} = 3\tilde{V}_{ln}^2/|Z_Y|$. Δ: $|S|_{3\phi} = 3\tilde{V}_{ll}^2/|Z_\Delta| = 9\tilde{V}_{ln}^2/|Z_\Delta|$.

Per unit. One base power S_b for the network, three-phase, typically 100 MVA; one base voltage V_b per zone, line-to-line, nominal. pu = actual/base; scales magnitues only and works in polar and rectangular forms. Single-phase $I_b = S_b/V_b$, $Z_b = V_b^2/S_b$. Three-phase $V_{b,ln} = V_{b,ll}/\sqrt{3}$, $I_b = S_b/(\sqrt{3}V_{b,ll})$, $Z_b = V_{b,ll}^2/S_b$; Base change: $Z_{pu,new} = Z_{pu,old}\,(V_{b,old}/V_{b,new})^2\,(S_{b,new}/S_{b,old})$. In pu, $|V_{ln}| = |V_{ll}|$ and $S_\phi = S_{3\phi}$: the bases carry the $\sqrt{3}$ and the 3. Across a transformer, set the other side's V_b by its line-to-line ratio; then Z_{pu} is the same on both sides and the ideal transformer drops out.

4 Power flow and admittance matrices

Admittance matrix. Recipe: number the nodes, ground as reference; generators as Norton current injections I_k; impedance loads and line charging as shunt admittances to ground; series impedances as $y_{km} = 1/Zkm$; KCL at each node in node voltages, $I_k = \sum_m Y_{km}V_m$; so $I = YV$ and solve for V in complex arithmetic; branch current $y_{km}(V_k - V_m)$. Y_{kk}: sum of all admittances touching node k, series and shunt. Y_{km}: minus the series admittance between k and m; zero if none. Y is symmetric and is singular without a shunt. $Y = A^\top \operatorname{diag}(y_{\text{series}})A + \operatorname{diag}(y_{\text{shunt}})$, A the branch-to-node incidence matrix.

Power flow. $S_k = V_k I_k^* = V_k\sum_m Y_{km}^* V_m^*$, generation minus load. With $V_k = \tilde{V}_k\angle\phi_k$, $Y_{km} = |Y_{km}|\angle\delta_{km}$: $P_k = \sum_m \tilde{V}_k\tilde{V}_m|Y_{km}|\cos(\phi_k - \phi_m - \delta_{km})$. Each bus: P, Q, $\tilde{V}$, ϕ; $2N$ equations, $4N$ unknowns. PQ (load): P, Q given. PV (generator): P, $\tilde{V}$ given. Slack (one): $\tilde{V}$, $\phi = 0$ given; supplies remaining P including P_{loss}. Solve: Newton on $x = [\phi$ (PQ, PV); $\tilde{V}$ (PQ)] with mismatch $f(x) = [P_k(x) - P_k^{given};\ Q_k(x) - Q_k^{given}]$ at those buses: $x \leftarrow x - J^{-1}f(x)$ from $\tilde{V} = 1$, $\phi = 0$. $J = [\partial P/\partial\phi,\ \partial P/\partial\tilde{V}\ ;\ \partial Q/\partial\phi,\ \partial Q/\partial\tilde{V}]$, by differentiating the P_k, Q_k sums. Then slack P, Q and PV-bus Q from their equations. $P_{loss} = \sum_k P_k = \sum_{(k,m)\in\text{lines}}|I_{km}|^2 R_{km}$, with $I_{km} = y_{km}(V_k - V_m)$.

5 Power line models

Models. Per unit length: series r, x [Ω/km]; shunt b [S/km], line charging, capacitive. Length ℓ: $Z = (r + jx)\ell$, $Y = jb\ell$. Short line: Z only. π model: Z in series, $Y/2$ to neutral at each end. All values per phase; the line is one branch of the per-phase circuit. Ampacity: maximum safe $|I|$.

Setup. Sending end S (source), receiving end R (load): V_S, I_S, V_R, I_R, all line-to-neutral and line current. Rated

voltage: $\tilde{V}_R$ at nominal, given as V_{ll} unless stated. Full load: I_R from the rated $|S|$ and pf at V_R; no load: $I_R = 0$. Solve from R back to S. Short line: $I_S = I_R$, $V_S = V_R + I_R Z$, $P_{loss} = 3|I_R|^2 R$. π model: $V_S = V_R + (I_R + V_R Y/2)Z$, $I_S = I_R + V_R Y/2 + V_S Y/2$. $P_{loss} = P_S - P_R$, with $P_S = 3\,\mathrm{Re}(V_S I_S^*)$, $P_R = 3\,\mathrm{Re}(V_R I_R^*)$. $VR = (|V_{R,NL}| - |V_{R,FL}|)/|V_{R,FL}|$ at fixed V_S; short line $V_{R,NL} = V_S$, π model $V_{R,NL} = V_S/(1 + ZY/2)$.

6 Magnetism and magnetic circuits

Magnetism. Magnetic field intensity H [A/m]. Permeability $\mu = \mu_r \mu_0$ [H/m]; $\mu_0 = 4\pi \times 10^{-7}$ H/m (air). Magnetic flux density $B = \mu H$ [T = Wb/m^2]. Magnetic flux $\Phi = BA$ [Wb] through a cross-section of area A [m^2]. Flux linkage $\lambda = N\Phi$ [Wb·turn] for a coil of N turns. Faraday: $v = d\lambda/dt = N\, d\Phi/dt$ [V]. Ampère: $\oint H\, dl = I_{enc}$, the current passing through the loop formed by the path. For the mean core path of length l [m] with uniform H, and a coil of N turns carrying i [A] threading the loop: $Hl = Ni$. Ni is the magnetomotive force (MMF) F [A·turn].

Magnetic circuit. Electric $\iff$ Magnetic: EMF V [V] $\iff$ MMF $F = Ni$ [A·turn]; current I [A] $\iff$ flux Φ [Wb]; resistance R [Ω] $\iff$ reluctance $\mathcal{R} = l/(\mu A)$ [A/Wb], for a segment of length l, area A, permeability μ; KVL $\iff$ $\sum F - \sum \mathcal{R}\Phi = 0$ around a loop (Ampère); KCL $\iff$ $\sum \Phi = 0$ at a junction (flux continuity); Ohm's law $V = IR$ $\iff$ $F = \Phi\mathcal{R}$; series and parallel combine like resistance. Coil = MMF source of value Ni, direction by the right-hand rule. One $\mathcal{R}$ per segment of distinct l, μ, or A. Air gap: $\mathcal{R}_{gap} = l_{gap}/(\mu_0 A)$ dominates, since $\mu_0 \ll \mu_{core}$.

Inductance. Coil of N turns on a single core of length l, area A: $L = \lambda/i = (N\Phi)/i = (N(BA))/i = (N((\mu H)A))/i = (N((\mu(Ni/l))A))/i = N^2/\mathcal{R}$ [H]. Several segments: $L = N^2/\mathcal{R}_{total}$, with $\mathcal{R}_{total}$ seen by the coil.

Saturation. B cannot exceed B_{sat} anywhere in the core. Procedure: $F = Ni_{peak}$; Φ from the magnetic circuit; $B_k = \Phi_k/A_k$ in each segment k; $B_{sat} \geq \max_k B_k$, in the smallest A_k carrying the largest Φ_k.

Losses. Core, eddy: flux induces voltage in the core, voltage drives current, current heats; $\propto f^2 B^2$; fix with laminations and silicon steel. Core, hysteresis: area of the B–H loop per cycle; $\propto f \times$ area; fix by material. Winding, skin: AC current crowds to the surface; fix with Litz wire. Winding, proximity: one conductor's field induces eddy currents in its neighbors, worse with more layers; fix with fewer or interleaved layers, Litz wire.

7 Transformers

Two windings on one core, N_1 turns on the primary and N_2 on the secondary. Faraday on the primary, $V_1 = j\omega N_1 \Phi$, fixes the core flux Φ. The same Φ links the secondary, so $V_2 = j\omega N_2 \Phi$ and $V_1/N_1 = V_2/N_2$, with or without a load. A load draws I_2; its MMF $N_2 I_2$ would change Φ, so the primary draws the I_1 that cancels it. Dot: current into the dotted terminal of either winding drives flux the same way around the core. Define I_1 into the primary dot and I_2 out of the secondary dot; then V_1, V_2 are both + at the dots and MMF balance is $N_1 I_1 - N_2 I_2 = \mathcal{R}\Phi$. Autotransformer: one winding with a tap; primary and secondary share turns. Tap changer: moves the tap to change N_1/N_2 for voltage control.

Ideal. $\mu \to \infty \implies \mathcal{R} \to 0 \implies N_1 I_1 = N_2 I_2$. Turns ratio $a = N_1/N_2$, so $V_1 = aV_2$, $I_1 = I_2/a$, and $S_1 = V_1 I_1^* = S_2$.

Equivalent circuit (nonideal). Refer an impedance to either side: $Z_{eq2} = (V_1/a)/(aI_1) = Z_{eq1}/a^2$ and $Z_{eq1} = a^2 Z_{eq2}$. Shunt branch, on one side: magnetizing inductance L_m (energy stored in core) and core-loss resistance R_c (eddy + hysteresis). Series branch, on each side: winding resistance R_1, R_2 and leakage reactance X_1, X_2. Circuit for problems: primary terminals $\to (R_c \parallel jX_m) \to Z_{eq1} \to$ ideal a:1 $\to$ secondary terminals. Both tests apply a voltage and measure $\tilde{V}$, $\tilde{I}$, P at the primary terminals. Open-circuit test (secondary open, rated V_{oc} applied at the primary terminals; measure $\tilde{V}_{oc}$, $\tilde{I}_{oc}$, P_{oc}): $I_2 = 0$, so no current in Z_{eq1} and V_{oc} is across the shunt branch. $S_{oc} = \tilde{V}_{oc}^2 Y_{\mathrm{sh}}^*$ with $Y_{\mathrm{sh}} = 1/R_c - j/X_m$ gives $R_c = \tilde{V}_{oc}^2/P_{oc}$ and $X_m = \tilde{V}_{oc}^2/Q_{oc}$. Short-circuit test (secondary shorted, V_{sc} applied at the primary terminals; measure $\tilde{V}_{sc}$, $\tilde{I}_{sc}$, P_{sc}): the shunt branch is treated as open, so I_{sc} flows in Z_{eq1} alone. $S_{sc} = \tilde{I}_{sc}^2 Z_{eq1}$ gives $R_{eq1} = P_{sc}/\tilde{I}_{sc}^2$, $|Z_{eq1}| = \tilde{V}_{sc}/\tilde{I}_{sc}$, $X_{eq1} = \sqrt{|Z_{eq1}|^2 - R_{eq1}^2}$.

Solving. Efficiency $\eta = P_{\mathrm{out}}/(P_{\mathrm{out}} + P_{\mathrm{core}} + P_{\mathrm{copper}})$. $P_{\mathrm{core}} = P_{oc}$, constant at rated voltage. $P_{\mathrm{copper}} = \tilde{I}_1^2 R_1 + \tilde{I}_2^2 R_2 = \tilde{I}_2^2 R_{eq2}$. Voltage regulation VR: $V_{2,NL} = V_1/a$ and $V_{2,FL} = V_1/a - I_2 Z_{eq2}$ at the given load; $VR = 0$ for an ideal source. Leading pf: the component of $I_2 Z_{eq2}$ along $V_{2,FL}$ can be negative, so VR can be negative.

Three-phase. Three single-phase transformers, each side Y or Δ; bank rating $S_{3\phi} = 3S_{\mathrm{transformer}}$. Winding quantities: Y side $V_w = V_{ln}$, $I_w = I_{\mathrm{line}}$; Δ side $V_w = V_{ll}$, $I_w = I_{\mathrm{line}}/\sqrt{3}$. Per-transformer turns ratio $a = V_{1,w}/V_{2,w}$; line-to-line ratio $V_{1,ll}/V_{2,ll} = a$ (Y–Y, Δ–Δ), $a/\sqrt{3}$ (Δ–Y), $\sqrt{3}a$ (Y–Δ). Δ–Y and Y–Δ shift voltages and currents by 30° between sides;

magnitudes and powers unaffected. Procedure: convert line to winding quantities and $S_\phi = S_{3\phi}/3$; solve the single-phase problem on one transformer; convert back; add the 30° only if a phasor is needed relative to the other side.

8 Machines

Rotor: rotating part. Stator: fixed part. Field winding: makes the main flux from DC current i_f or a permanent magnet. Armature winding: has the EMF induced in it; its current i_a carries the converted power, from the supply in a motor and to the load in a generator. DC: field on the stator, armature on the rotor. Synchronous: field on the rotor, armature on the stator. Motor: electrical in, mechanical out. Generator: the reverse. $E_{\text{electric}} = E_{\text{mech}} + E_{\text{field}} + E_{\text{loss}}$. Four facts: current in a wire makes a field (transformer primary); a wire carrying i in field B feels $\vec{F} = i\,\vec{l} \times \vec{B}$ (motor); a changing field makes a voltage in a coil (transformer secondary); a wire moving at $\vec{v}$ in field B has EMF $e = (\vec{v} \times \vec{B}) \cdot \vec{l}$ (generator). Left-hand rule, motor: pointer B, middle i, thumb F.

DC machines. Stator: field, fixed flux from a permanent magnet or DC field winding. Rotor: armature, fed DC through brushes; the commutator reverses each coil's current every half turn so torque keeps one direction. (+) cheap drive, stable. (−) commutator wear.

Circuit: terminals → R_a → L_a → back EMF $E = k_e\omega$, so $V = R_a i_a + L_a\, di_a/dt + k_e\omega$. Steady state ($i_a$ constant) drops the L_a term; everything below assumes it. Motor (i_a flows terminal → R_a → E): $V = R_a i_a + k_e\omega$. Generator (i_a flows E → R_a → terminal): $V = k_e\omega - R_a i_a$. Back EMF constant $k_e = (V - i_a R_a)/\omega$ [V·s/rad], from a no-load test. Torque constant k_t [N·m/A] in $T = k_t i_a$. Power balance $P_{\text{mech}} = E i_a = T\omega \implies k_e = k_t$, so one test gives both. $P_{\text{in}} = V i_a = E i_a + i_a^2 R_a$, $\eta = P_{\text{out}}/P_{\text{in}}$. Torque–speed: $\omega = V/k_e - T R_a/(k_e k_t)$, a line from no-load speed $\omega_0 = V/k_e$ ($T = 0$) to stall torque $T_0 = k_t V/R_a$ ($\omega = 0$). Procedure: given V, R_a, $k_e = k_t$ and either T or ω, the line gives the other; $i_a = T/k_t$; then powers.

Synchronous machines. Stator: armature, three-phase winding; its currents make a field rotating at ω_s and carry the AC power. Rotor: field winding with DC i_f through slip rings (or a permanent magnet); its flux locks to the rotating field, so the shaft turns at ω_s. p pole pairs: $\omega_s = \omega_e/p = 2\pi f_e/p$ [rad/s], $n_s = 60 f_e/p$ [rpm], since the stator field advances one pole pair, $1/p$ of a turn, per electrical cycle. Starting: at standstill the torque alternates at f_e and averages zero. A squirrel cage on the rotor gives induction torque to start and carries no current once synchronized (no slip); or a VFD ramps f_e from zero. (+) pf set by i_f; speed fixed by f_e. (−) not self-starting; needs a DC field supply. Magnetic circuit: $(N_f i_f \to \mathcal{R}_{\text{gap}} \to \mathcal{R}_{\text{rotor}} \to \mathcal{R}_{\text{gap}} \to N_f i_f) \parallel (\mathcal{R}_{\text{stator}} \parallel \mathcal{R}_{\text{stator}})$. Per-phase circuit, generator (I_a out of the stator terminals): EMF $E_a \to R_s \to jX_s \to$ terminal V_a, so $V_a = E_a - (R_s + jX_s)I_a$. Problems set $R_s = 0$; everything below assumes it. Motor (I_a into the stator terminals): $V_a = E_a + jX_s I_a$. $E_a = k_f i_f \omega_e \angle\delta = (L_f/\sqrt{2})\, i_f \omega_e \angle\delta$: magnitude set by i_f; power angle $\delta = \phi_{E_a} - \phi_{V_a}$ for a generator, $\phi_{V_a} - \phi_{E_a}$ for a motor, so $\delta > 0$ in both. $P_{3\phi} = 3\tilde{V}_a \tilde{E}_a \sin\delta / X_s$, $Q_{3\phi} = 3\tilde{V}_a(\tilde{E}_a \cos\delta - \tilde{V}_a)/X_s$; delivered by a generator, absorbed by a motor. Procedure, given $|S_{3\phi}|$, pf, $\tilde{V}_{ll}$, X_s: $I_a = (|S_{3\phi}|/(3\tilde{V}_a))\angle(-\theta)$ with θ from pf; then $E_a = V_a + jX_s I_a$ (generator) gives $\tilde{E}_a$, so i_f, and δ. Procedure: given $\tilde{E}_a$, $P_{3\phi}$, $\tilde{V}_{ll}$, X_s, get δ from the P equation; then $I_a = (E_a - V_a)/(jX_s)$ and $Q_{3\phi}$. Torque–speed: vertical line at ω_s. Torque–δ: $T = P_{3\phi}/\omega_s = 3\tilde{V}_a \tilde{E}_a \sin\delta/(X_s \omega_s)$, a sine, max at $\delta = 90°$, unstable past it. $T = (\pi/2)\, p\, \Phi_r F_f \sin\delta$ with air-gap flux per pole Φ_r and field MMF $F_f = N_f i_f$; raise T by Φ_r (limited by B_{sat}) or F_f (limited by field heating).